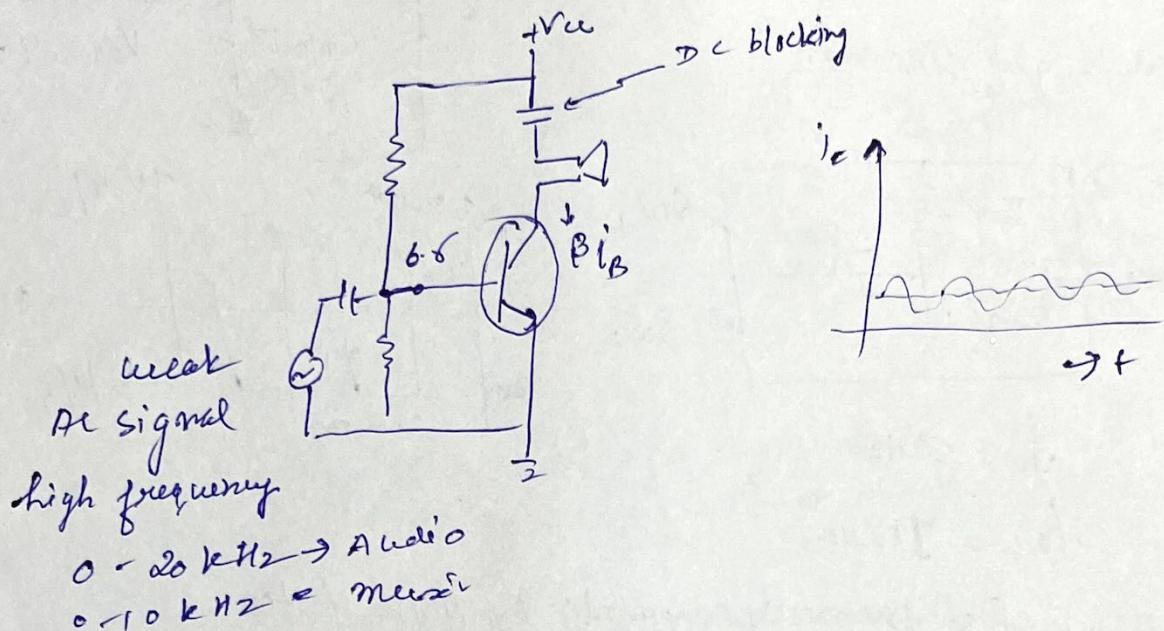


# EED 306 : Power Electronics

- Earth current  $> 20 \text{ mA} \Rightarrow$  Trip. supply (ELCB)
- Application  $\Rightarrow$  HVDC
- Basic Amp.  $\Rightarrow$  On/Off, PE  $\Rightarrow$  S.M.P.S
- Power electronics  $\Rightarrow$  Few watts to several mega watts.  
work in switched mode.



Average  $\leftarrow R_{\text{thermal}} b/r \text{ junction core}$   $\square$  Semiconductor device


$$\theta_C = R_{\text{thermal}} \times \text{Watts}$$

(temp. rise)  $\hookrightarrow \theta_C / \text{watt}$

~~Ambient temp  $\Rightarrow 50^\circ\text{C}$~~   $\rightarrow$  outside the device  
 $T_j < 110^\circ\text{C}$   $\rightarrow$  difference  $= 60^\circ\text{C}$

$$SI \Rightarrow T_j < 150^\circ\text{C}$$
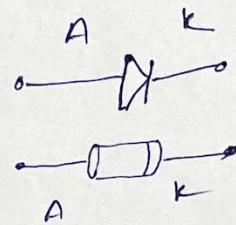
$$^\circ\text{C/watt} = 0.4^\circ\text{C/watt}$$



let  $R_{\text{thermal}} \Rightarrow 10^\circ\text{C/watt}$  { by manufacturer }

$$10^\circ\text{C/watt} \times P = 60^\circ$$


$P = 6 \text{ W}$  is the max<sup>n</sup> power that can be dissipate in the device or switch

Cut off  $\Rightarrow i_B \approx 0$   $i_{SW} \approx 0$

Active  $\Rightarrow i_B \rightarrow \frac{1}{R_E}$  Power flow from C to E


Saturation  $\Rightarrow i_B > \frac{i_c}{\beta} \Rightarrow V_{CE} = 0.2V$

$V_{SW} \approx 0$

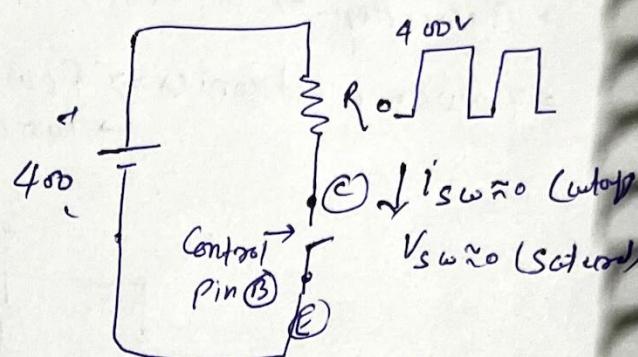


Q How to get sine wave?

M

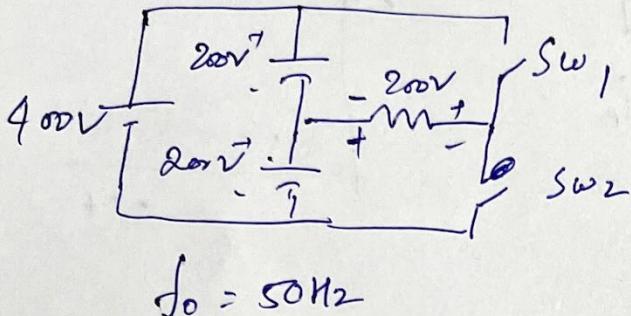

$f_{SW} = 10\text{kHz}$


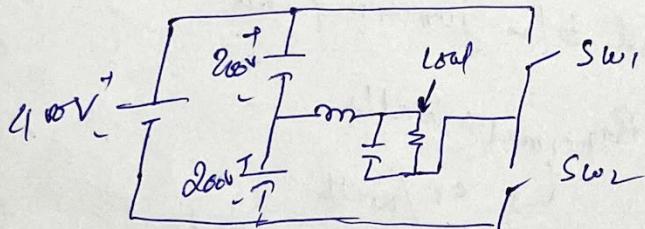
Block high frequency components by using filter


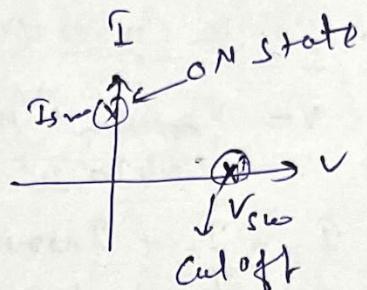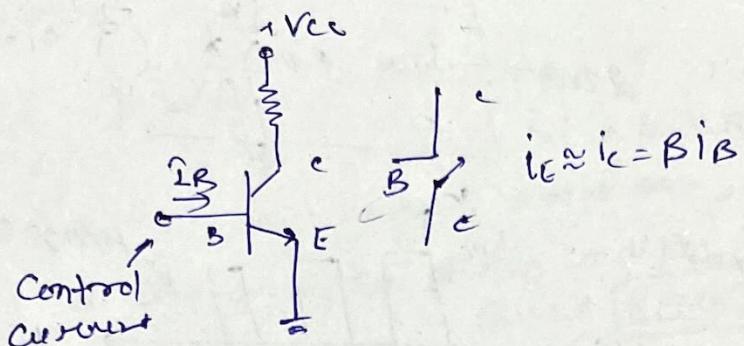
## Essential power conditioning CKAB:


Electrical Power (available form)  $\Rightarrow$  [Power Conditioning Circ]  $\Rightarrow$  Electrical Power (required by user)

AC / DC  
fixed or variable  
magnitude of  
variable / fixed  
low / high



Saturation  $V_{sw} \approx 0V \Rightarrow 0.2-0.3V \Rightarrow$  for signal diode  
cutoff  $I_{sw} \approx 0A \Rightarrow 2-3V \Rightarrow$  for power diode

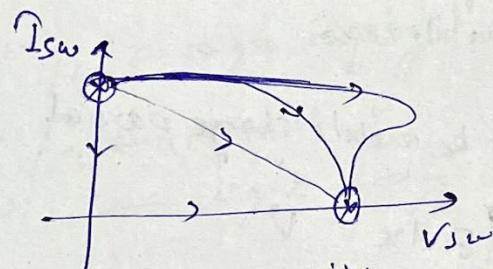- Thermal resistance  $\rightarrow$  Junction  $R_{th,j,c}$   $\rightarrow$  arm and  $R_{th,c,a}$   $\rightarrow$  single
- Approp 140°C
- As Temp.  $\uparrow$  Si crystal become polycrystal from monocrystalline
- Nowadays we use silicon carbide  $\Rightarrow$  600°C limit



Trajectories of switch from ON to OFF condition.

- If  $I_{sw}$  is  $\uparrow \Rightarrow$  Power  $\uparrow$
- when  $S_w \rightarrow ON \Rightarrow$  conduction loss } at junction
- "  $S_w \rightarrow ON$  to OFF or OFF to ON  $\Rightarrow$  switching loss }

A + junction

$$\Delta T = R_{th} \times \text{watts}$$

Ans.  
Junction  
 $R_{th,c,a}$


- In small motors  $R_a$  is more than larger motors because wire is thinner.
- The sparking in the switch during on and off condition due to inductance.

### Buck Converter:


$$V_o = V_{\text{funders}} + V_{\text{harmonic}}$$

due to DC component

20V

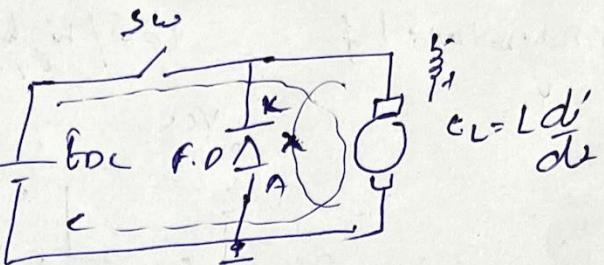

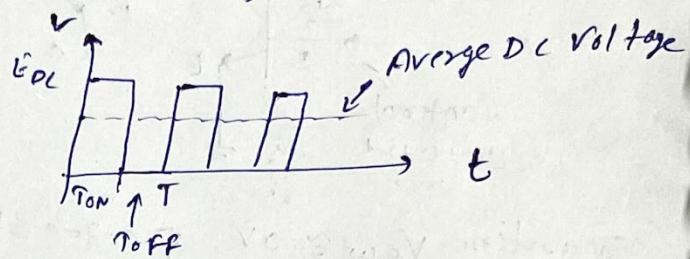- $I_o$ ,  $I_o + I_{\text{harmonic}}$   
due to DC component.




$$\frac{t_{0n}}{T} = D$$

$\alpha < D < 1$

$$V_{\text{drop}} = D E_d i$$

### Diode:

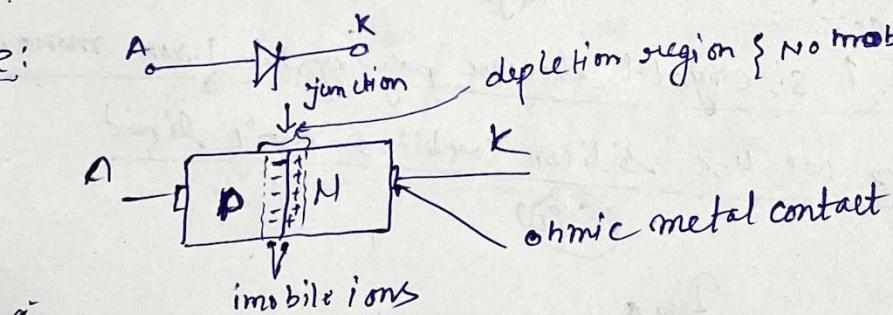


ion  $\Rightarrow$  too big to be mobile  $\&$  charge partial

$$\int E \cdot dx = V$$

$$V =$$

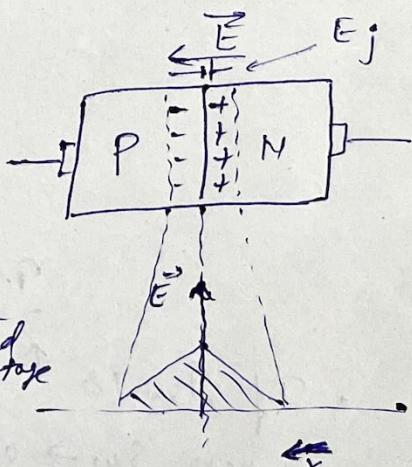
Signal level  $\Rightarrow 1A / 50V$   
Power elec.  $\Rightarrow 5000W / 10kV$



- As  $V_d \uparrow$ ,  $E_f \uparrow$  ∴ slope of  $E_f$  remains constant.

- ~~$D$~~  + the  $I_o$  will flow in reverse direction but only for short amount of time. as  $E_f = E_{ext}$   $I_o = 0$  if No current flow.

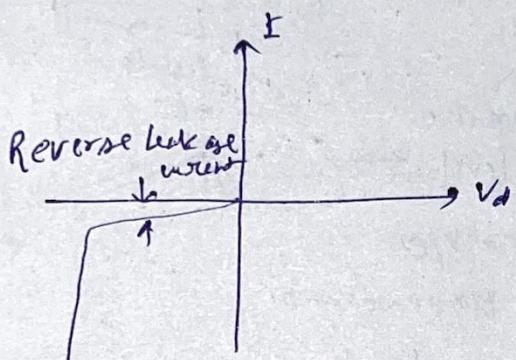- If  $E_{ext}$  in reverse kept on  $\uparrow V_d \uparrow$ , it will touch metal contact  $(I_o)$  will be very large & breakdown of diode occurs ⇒ This condition is called **Reach Through**







Steady state character

$$\textcircled{5} \rightarrow I_o^{\text{st}} / cc$$

doping  $\rightarrow 10^{18} - 10^{14} / cc$  ← high doping  
 $10^{14} - 10^{16} / cc$  ← normal "  
 $10^8 - 10^3 / cc$  ← light doping

- Thermally generated e-h pair mostly from Si. form PtoN movement of  $e^-$  in the opposite direction " h in " same direct.

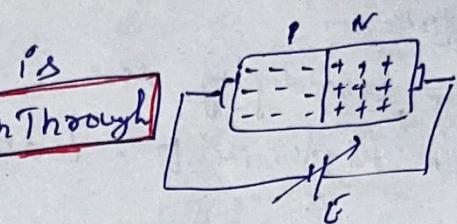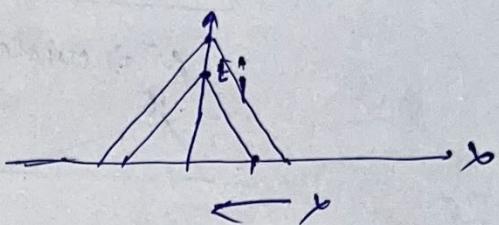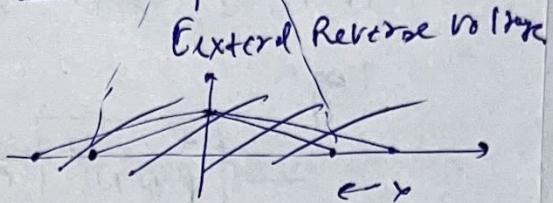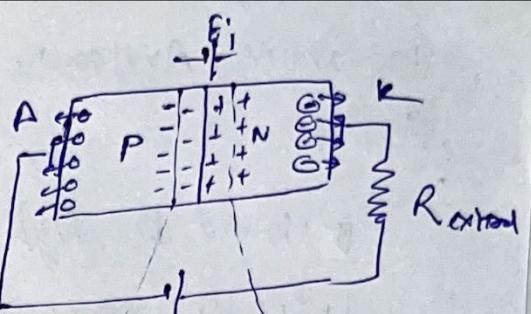NOTE: • Breakdown due to Reach through or Avalanche B/D



### Avalanche B/D

when  $E$  is too high force on  $e^-$  is high  $\vec{F} = e\vec{E}$   
 $e^-$  has high  $kT$  it will collide with other atom & create e-h pair & process continuous & there will be large amount of e-h pair &  $I_o$  will be large

from  $Si$

Called avalanche B/D



$\left. \begin{array}{l} E > 2 \times 10^5 V/cm \\ \text{oxinside Semiconductor} \end{array} \right\}$

To avoid Avalanche BLD we need to avoid high  $E$ .

$$\int E \cdot dx = V$$

or should be high as per application but  $E$  should be less. If one side is highly doped then slope will be less.

Logo:

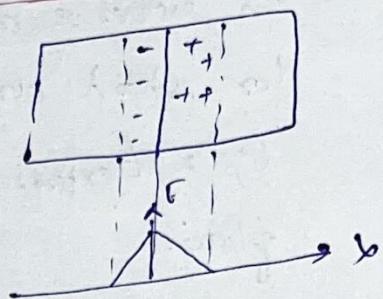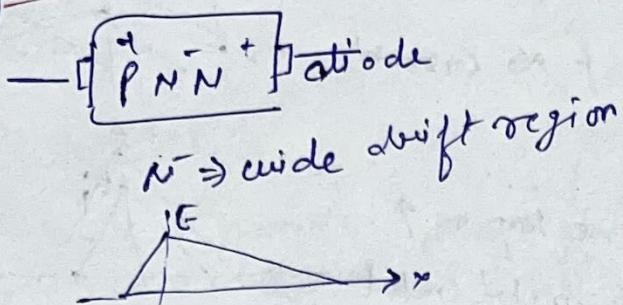

29/08/2022

- Less doping less  $E$  slope
- Higher the  $V$ , less is the doping




Drift region  
Highly resistive

Avalanche  
BLD level

$$E_{AV} = 2 \times 10^5 \text{ V/cm}$$

- Reverse current is function of temperature
- If photo bombardment is done on Junction  $e^-h$  pair may be induced

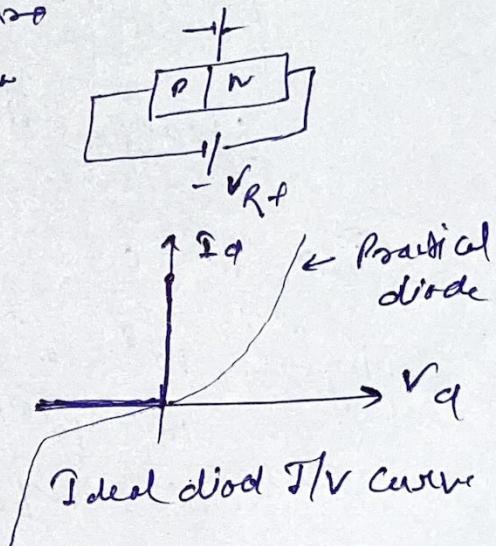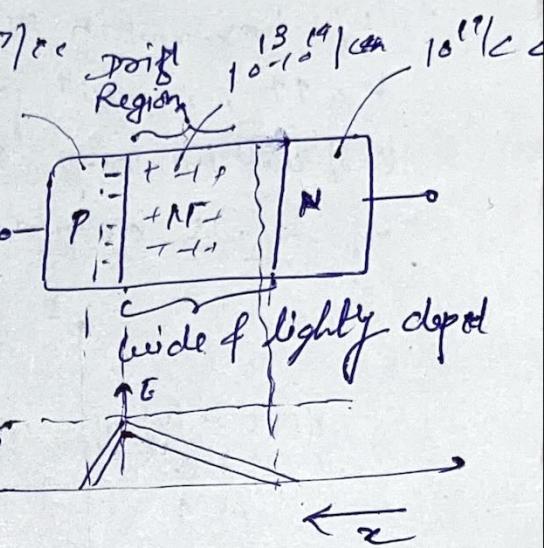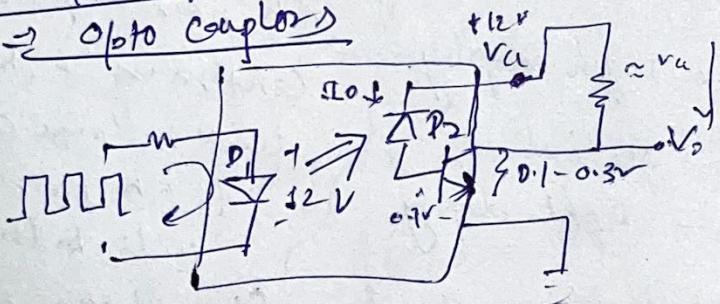Application of normal p-n Diode  
 $\Rightarrow$  opto couplers




$e^-h$  pair generated from Si because its density is high  
 $10^{27}/\text{cc}$  compared to impurity  $10^{13}-10^{19}/\text{cm}^3$

- $V_i \Rightarrow \text{high} \Rightarrow J \rightarrow oN \Rightarrow$  Emitter light  $\Rightarrow D_q \Rightarrow R.B.$  To flows, Transistor  $\Rightarrow oN \Rightarrow I_{C2} B^2 BE \Rightarrow$  drop in  $R_{C2} B^2 BR_C$
- $V_{Qc} \approx V_{CE} \text{ & } V_{op} \approx 0$
- $V_i \Rightarrow \text{low} \Rightarrow J \rightarrow oN \Rightarrow$  No condition of light  $\Rightarrow D_q \Rightarrow \text{off}, I_B = 0$   
 $I_C = 0, V_{RE} \approx 0, \text{ & } V_{op} = V_{CE}$
- In this connection R.B. Diode may take time to recombine after every operation
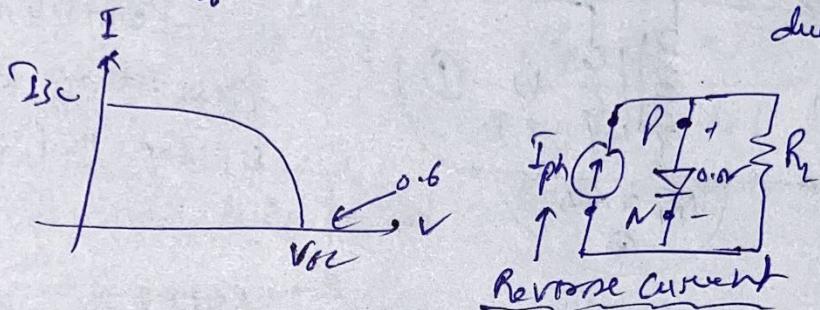
## ② Another $\Rightarrow$ PV cell

in OC condition  $I_{\text{diffusion}} = I_{\text{dark}} + I_{\text{20}}$  —  $\boxed{\frac{P = \frac{q}{e} \cdot A \cdot N}{I_{\text{dark}}}}$   
 due to  $P$




Power diode  
Drawback  $\Rightarrow$

$$\boxed{P \left[ \frac{T}{N} \right] n}$$

$\Delta T$   $\uparrow$   $\uparrow$   
~~high~~ due to Drift region



so high voltage drop in large resistors.

Conductivity modulation:

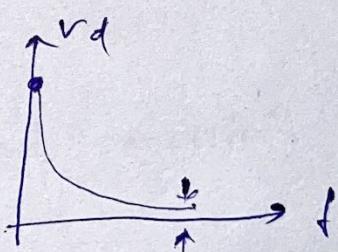




## Power Transistor

Lab 2

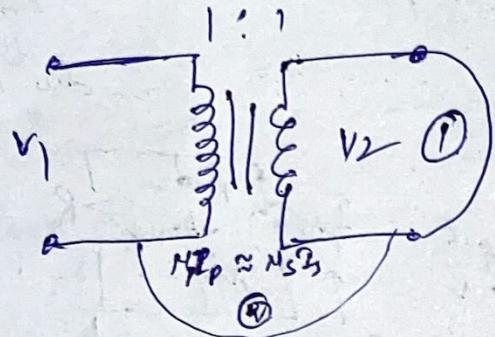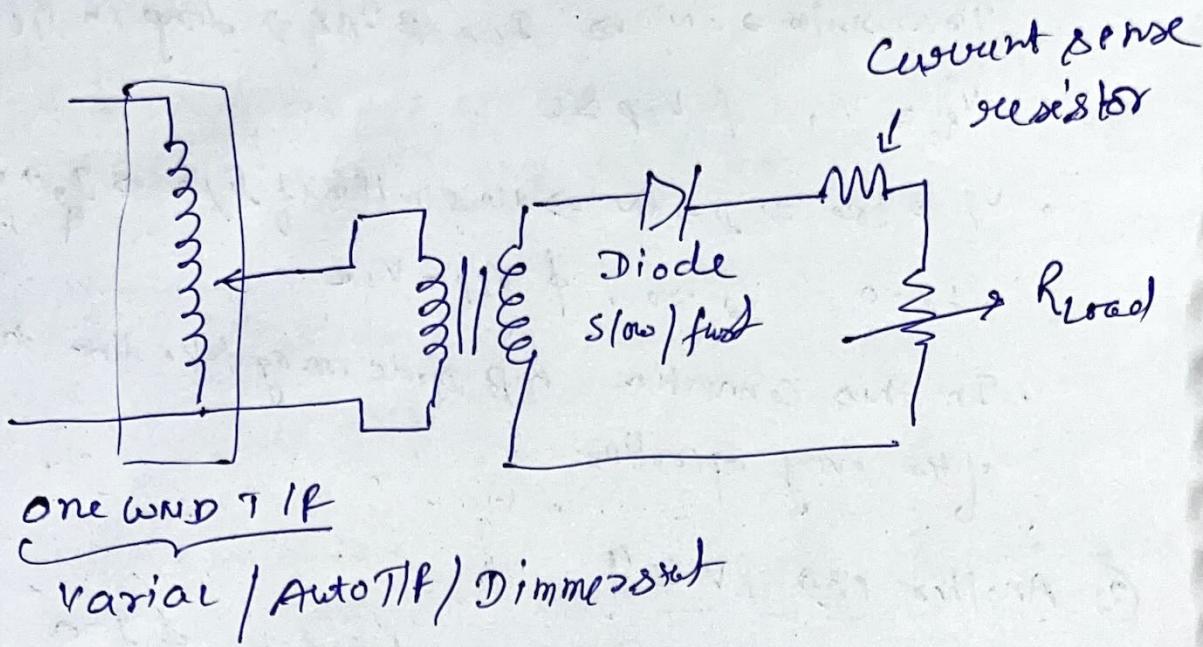

Connection ① or ② worst  
caused any damage in the TIP  
because V<sub>1</sub> & V<sub>2</sub> are floating voltage

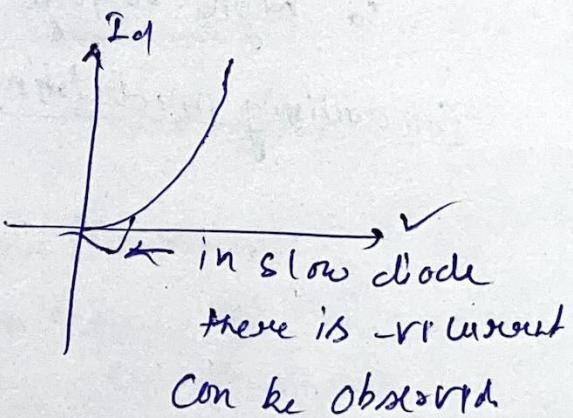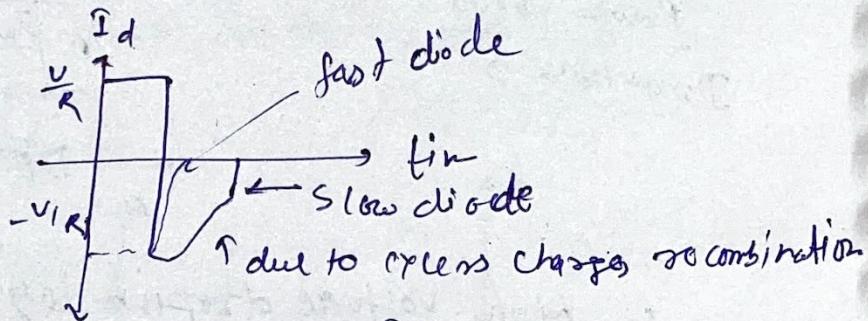
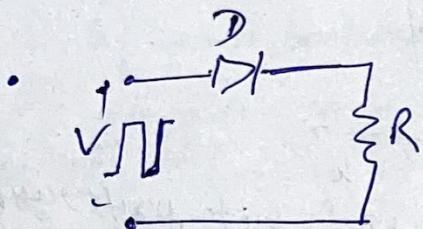
- Energy density =  $\frac{B^2}{2\mu_0}$   $\frac{\text{Energy}}{\text{Volume}}$



2/10/2022

- Power Transistor:

- Signal level transistor:

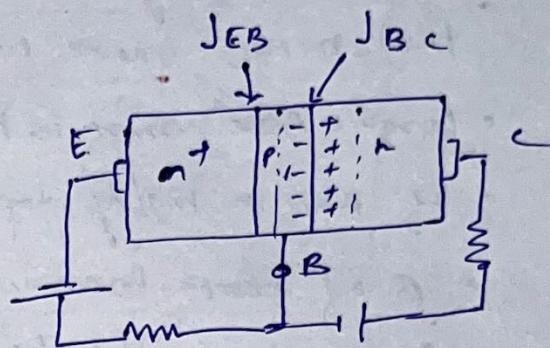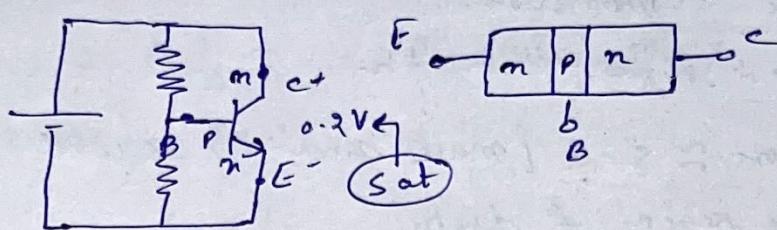

$I_E = \text{predominantly } B$  due to  $e^-$  flow from  $N^+$  to  $P$

(E) (B)

Base  $\Rightarrow$  Lightly doped & thin layer

$e^-$ s which enter B are swept to Collector region by  $E^+$

$$\alpha I_E = I_C \quad 0 < \alpha < 1$$

only for active mode

$$\frac{I_C}{I_B} = \frac{\alpha}{1-\alpha} = B = h_{FE} \approx 100$$

$$I_C = B I_B$$

$$I_B = (1 - \alpha) I_E$$

\* neglecting hole component of Base current.

- Saturation  $\Rightarrow$


$0.2\text{V}$  small voltage drop in Sat

- Power Transistor:


High Voltage rating

High Current rating

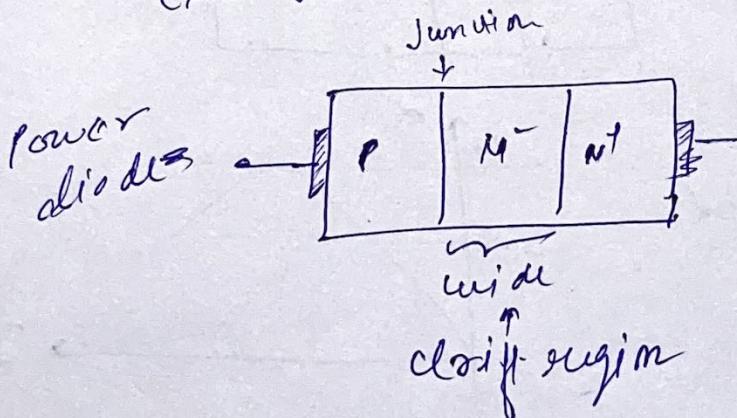
Ex- IM222, 60V, 0.8A { signal Transistor }



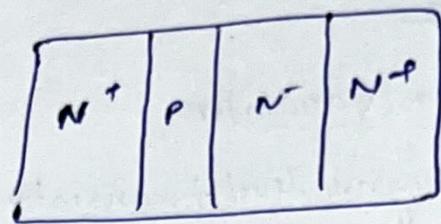- In power transistor, Base is a little wider than signal transistor.  
that means more width in  $V_{RB}$ .






- Larger Base area is the recombination
- If Base is highly doped  $I_{Bn}$  will be  $I_B$ .
- $\beta$  of power transistor  $\approx 5-6$  [much smaller] because of compromise with base region of doping.
- ✓ single Power Transistor will have high  $I_B$  for control so we use Darlington pair for operation
- $\alpha \uparrow \Rightarrow B_1, B_2, B_3$
- But higher Voltage drop. ( $0.9 + 0.6 + 0.5$ )

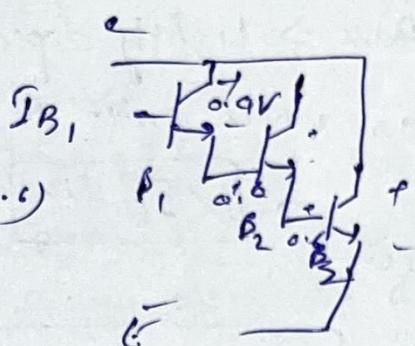

• 5/9/22

### • Thyristor:

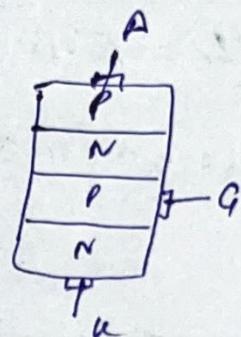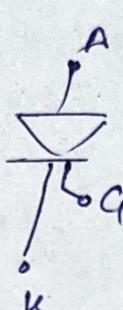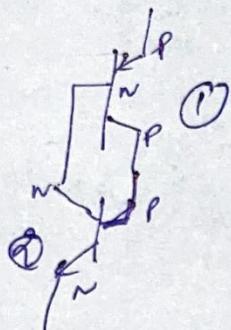



$$I_C \approx I_E$$

$$I_B = (1-\alpha) I_E$$

$$\frac{I_C}{I_B} \Rightarrow \beta = \frac{\alpha}{1-\alpha}$$

for  $\alpha > 0.5$ ,  $\beta > 1$

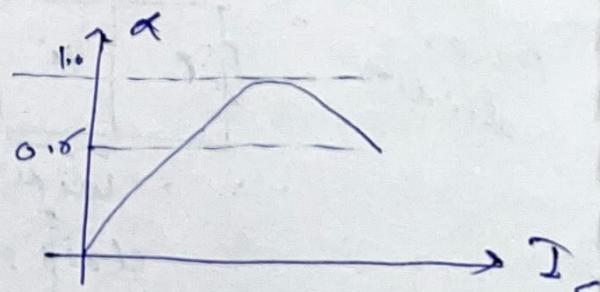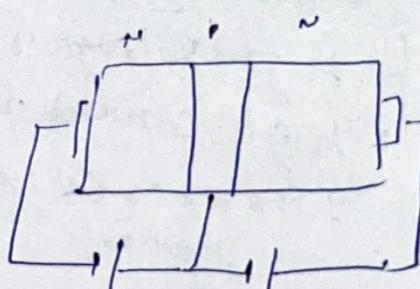- But for Si  $\alpha$  does goes beyond 0.5 easily




If 'B' of ① + ② are  $> 1.0$

$$\beta = \frac{I_C}{I_B}$$

$$I_{B_2} = I_{C_1}$$

if  $\beta_1 + \beta_2 > 1.0$   $I_{C_1} + I_{C_2}$  drop adding up

$$I_B \approx I_C$$

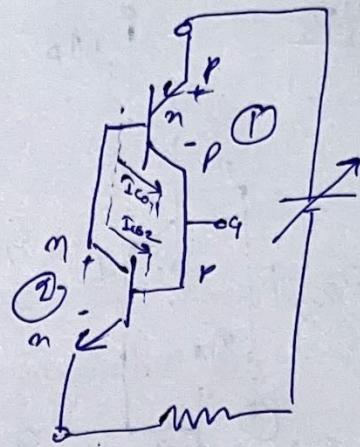

If  $I_B > \frac{I_C}{\beta}$  transistors enters into saturation Region

for  $I_B > \frac{I_C}{\beta}$  (in active region)

as  $I_C$  is provided at 'a'.

$$I_C = \beta I_B \uparrow$$


so current through transistors compound

$\uparrow$  if  $\beta$  will go beyond  $0.6 \beta$



$\beta$  go more than. Current starts to build up like feedback that will make it go saturation

$$I_{C_1} \uparrow \rightarrow I_{B_2} \uparrow \rightarrow I_{C_2} \uparrow \rightarrow I_{B_1} \uparrow \rightarrow I_{C_1} \uparrow$$

so both parallel currents become equal


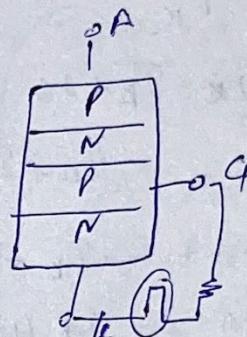


$$\beta > 6$$

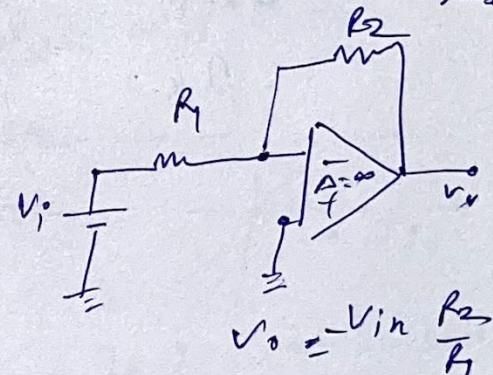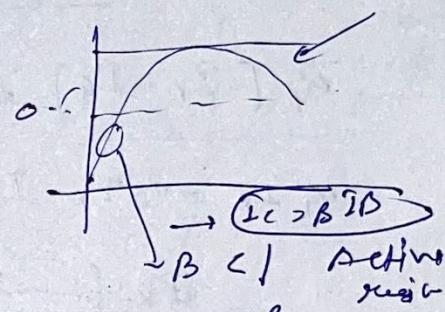

$$V_o = V_{in} \frac{R_2}{R_1}$$

7/9/22

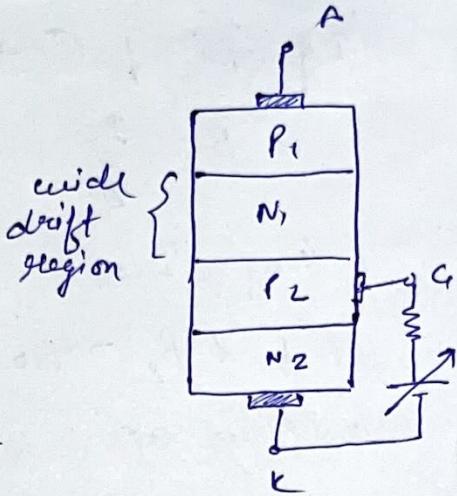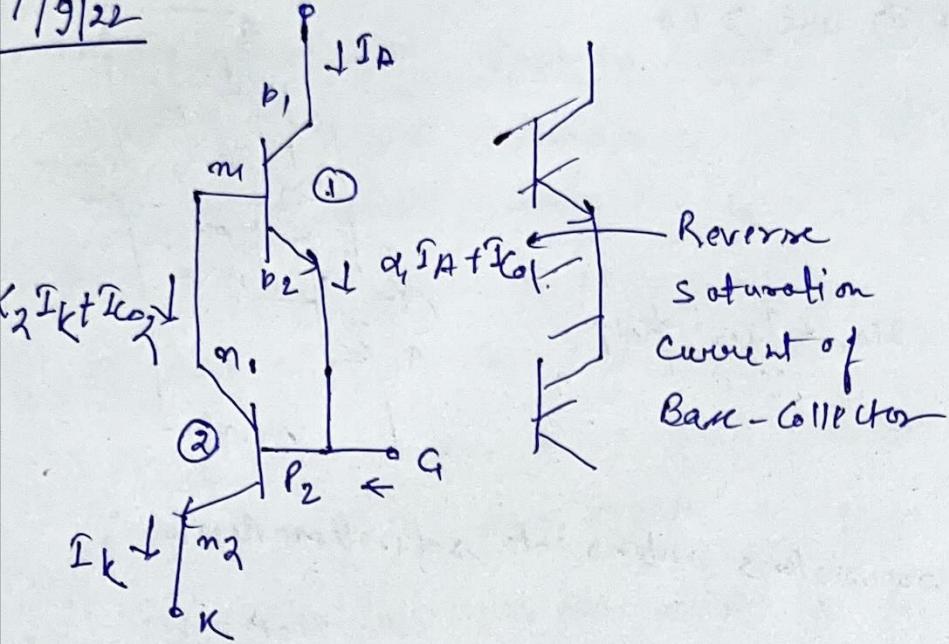

$$I_K = I_A + I_G$$

$$I_K = \alpha_1 I_A + I_{C01} + \alpha_2 I_K + I_{C02}$$

$$\alpha_1 I_A = I_K - \alpha_2 I_K - I_{C01} - I_{C02}$$

$$I_A = \frac{I_K (1 - \alpha_2) - (I_{C01} + I_{C02})}{\alpha_1}$$







$$\alpha_1 [I_K - I_G] = I_K - \alpha_2 I_K - (I_{C01} + I_{C02})$$

$$\alpha_1 I_K - \alpha_2 I_K - I_K = I_G \alpha_1 - (I_{C01} + I_{C02})$$

$$\underline{I_{K2}} = \frac{\underline{I_{C01} + I_{C02}}}{1 - \alpha_1 - \alpha_2} + \frac{\underline{I_G (1 - \alpha_1)}}{(1 - \alpha_1 - \alpha_2)} \quad B = \frac{I_C}{I_B} \approx \frac{I_B}{I_1} = \alpha_1 - \gamma_2$$

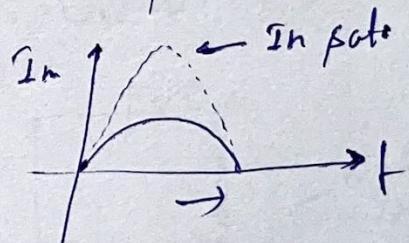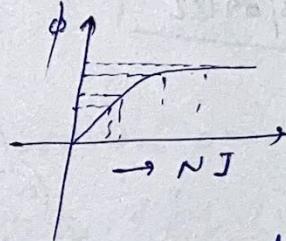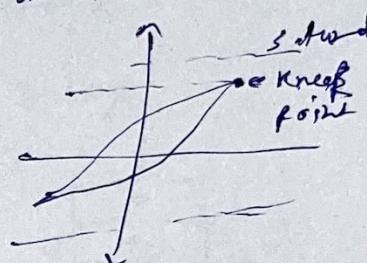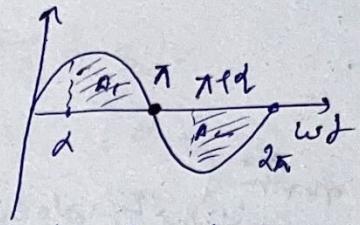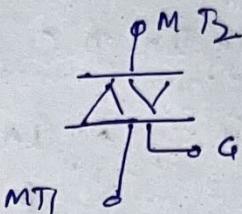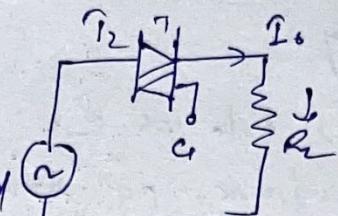
## TRIAC:

- It is more sensitive to +ve Gate current compared to -ve Gate current
- that means  $+ I_g \approx$  small magnitude required to turn on  
-  $I_g \approx$  comparatively larger magnitude required to turn off
- In SCR & TRIAC once turned on the current decided by  $R_L$ .
- triggering or firing: once TRIAC is turned on so that it starts to conduct is known as triggering or fire. O/P should not have dc component i.e.  $A_1 = A_2$  because if this o/p is sent to T/F, +  $I_{DC}$  in magnetising Branch BN curve may shift up or down depending on the direction of  $I_{DC}$ . If it may go into saturation As T/F is designed closer to knee point.
- If it is designed far from the knee point the  $A$  should be high & cost would be high
$$V = 4.44 f B_m \times A_c \phi$$
- In saturation to  $\top \phi$  by small value high  $I_{mag}$  is required.
- so magnetizing current become pulsating while  $\phi$  will still be sinusoidal.
- Harmonics  $\uparrow$ .
- TRIAC should be fired synchronously only


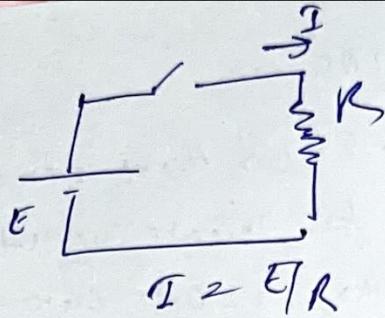
## In DC supply

- In DC,  $\alpha_{dc} \approx \pi/2$   
as previous eq do not apply




In ac if  $\alpha > 90^\circ$  Re load  $R_{avg} \neq \text{Half}$

$$= \frac{V_s}{\sqrt{2}} \quad R_{avg}$$





mean square =  $\frac{1}{2}$  of  $V_s$  at  $90^\circ$

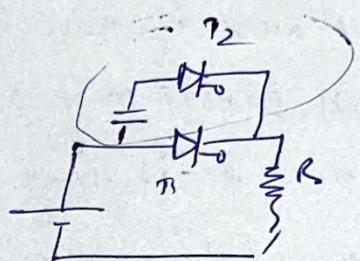- <sup>normal</sup> multimeter does not measure true RMS. [if do not use accurate]
- So we use TRUE RMS meter.




Commutation Ckt

03/09/22

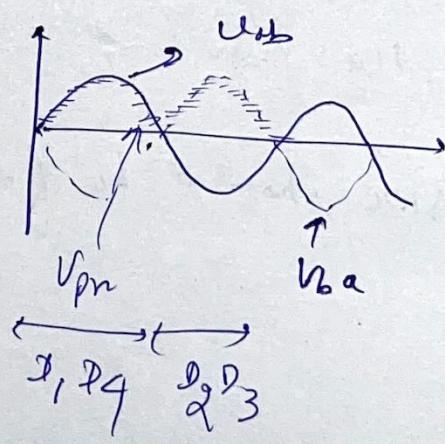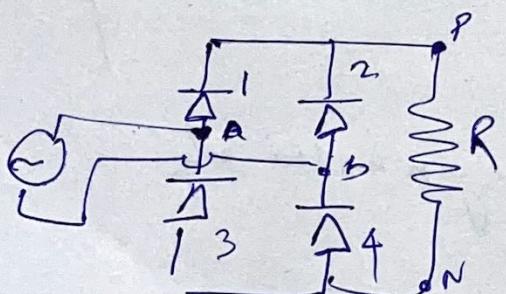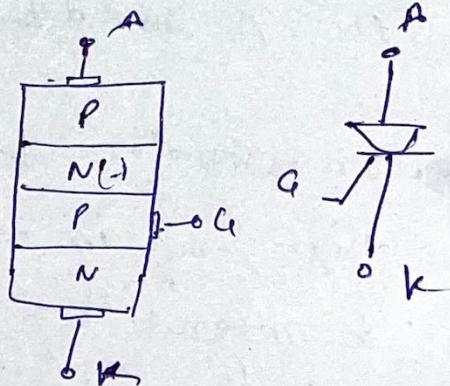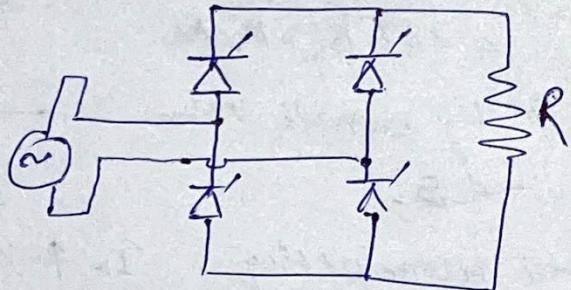

$$V_{pn\text{ avg}} = \frac{1}{\pi} \int_0^\pi V_m \sin \omega t dt$$
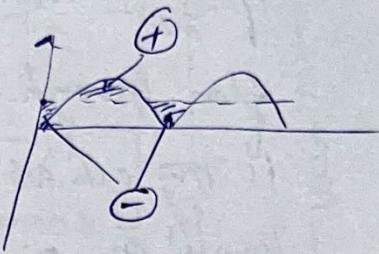
$$= \frac{V_m}{\pi} \left[ -\cos \omega t \right]_0^\pi$$





$$V_{pn\text{ avg}} = \frac{2V_m}{\pi}$$

(avg)

- Average of Ripple voltage  $\geq 0$  in Diode Bridge

- for 230 V, diode rating  $\Rightarrow V_{\text{diode}} = 230\sqrt{2} \approx 311 \text{ V}$

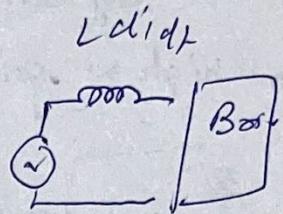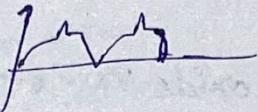
- for weak line spike may come due to change in load (ex. neighbour load)



- For SCR  $\Rightarrow$  Rating 1200 V  $\Rightarrow$  Peak forward Voltage & Peak Reverse Voltage


- Drift Region  $\Rightarrow$  wider & lightly doped

$$J_1 + J_3 \Rightarrow R_B$$

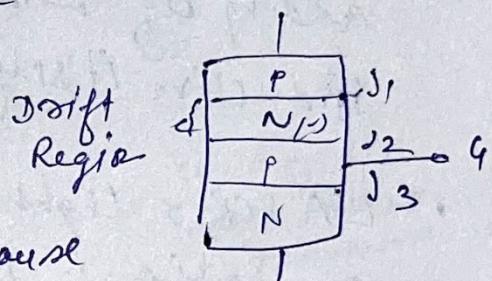

- $J_3$  blocks small portion of  $V_{RB}$  because doping is higher

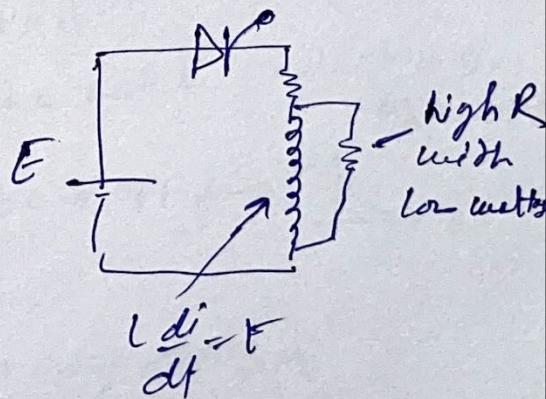{ It is a little advantage as if  $I_a$  is provided accidentally  
It may turn on but higher voltage is blocked by  $J_1$  }




- $\frac{dv}{dt}$  turn on:

if  $\frac{dv}{dt} \uparrow$  in F.B. Reverse current

flows through  $J_2$  momentarily

it may act as  $I_G$  and may


turn it on or unscheduled turn on.

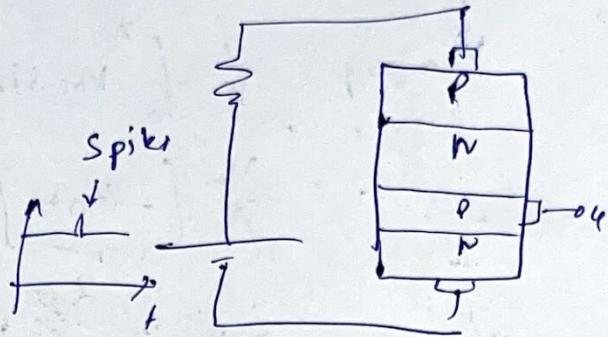

- It may occur in AC or dc supply by sudden change of load too.

- spike  $\Rightarrow$  high freq very compres (wt)

for high w spike  $\omega L > \omega_C$

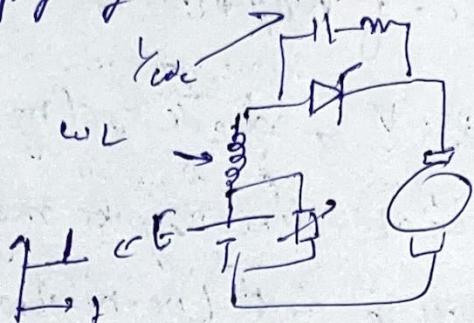


MOV (metal oxide varistor)

- To avoid false turn on  $\Rightarrow$  we provide snubber circuit   
 adding of  $C_m$  is not in general required as there is inductive itself.

- LASCR = light activated SCR.

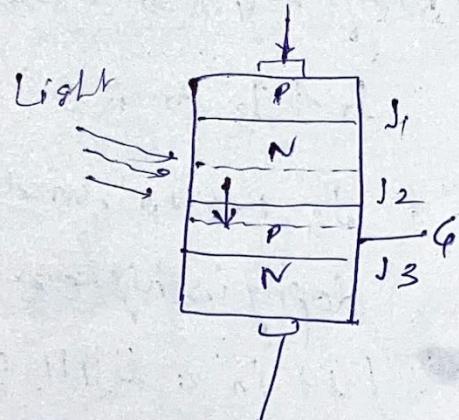Application - HVDC as rating is high so insulation requirement is also high



12/09/22

### • Thyristor turn-off

initially  $\Rightarrow$  discharge of Thyristor FB

- 1st  
- A.S. ThA  $\rightarrow$  on current path

$E \rightarrow C \rightarrow ThA \rightarrow RLL (load)$

as  $V_C^{(charged)}$  tends to E no current  $C'$

should flow in path b but due to load inductance, current will not be zero immediately.

Sparking occurs in similar manner in welding T/F. as inductive effect.

$e = L \left( \frac{di}{dt} \right) \Rightarrow$  it must be large to produce high voltage to ionise the air around the switch

•  $\frac{di}{dt} = -ve$  (decaying)

now due to current by Z a little extra

voltage come across C  $\Rightarrow E + \Delta E + V_{load} = (E - V_0)$

so D  $\rightarrow$  F.B.

(F.O.)

• so two path for inductor

① Thyristor C


② " PD(L)

current for thyristor & current through ThA will be reduced to 0.  $I_{ThA} = 0$  P.R.



{ if load  $\Rightarrow R$  as  $V_C = E$   $I_{Th} = 0$  if ThA  $\Rightarrow$  off }  $\Rightarrow$   $i_C$  vs t

• now C is charged to E.

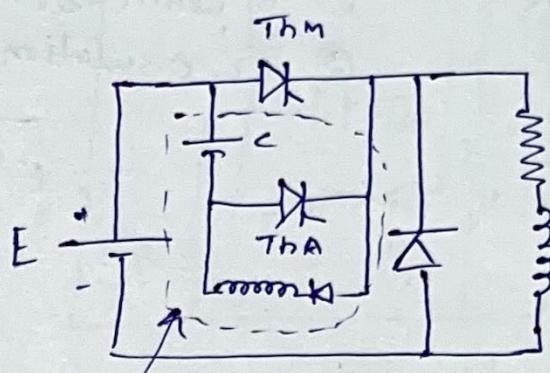This is the main requirement for turning off them



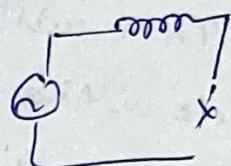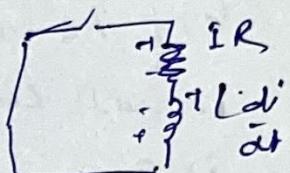
Thyristor DC/DC chopper  
Commutation Ckt for ThM



welding t/f  
large leakage  
Inductance

- When  $T_{HM} \rightarrow 0N$

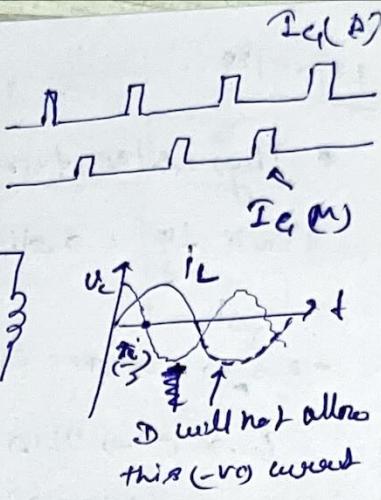- ① E connected to L + D
- ② LC oscillation occurs.



So after charge storage of  $V_L$ , it will stop.

After charge storage.

$$T_{HA} \rightarrow FB$$


& if  $I_A$  is greater than  $T_{HA}$  it will conduct.

if  $I_A > 0$ ,  $T_{HA} \rightarrow ON$

$T_{HM}$  will be  $R_B$

• also will have to keep  $T_{HM} \neq R_B$  for some time so that charge in  $T_{HM}$  can recombine otherwise it will be turn off failure.

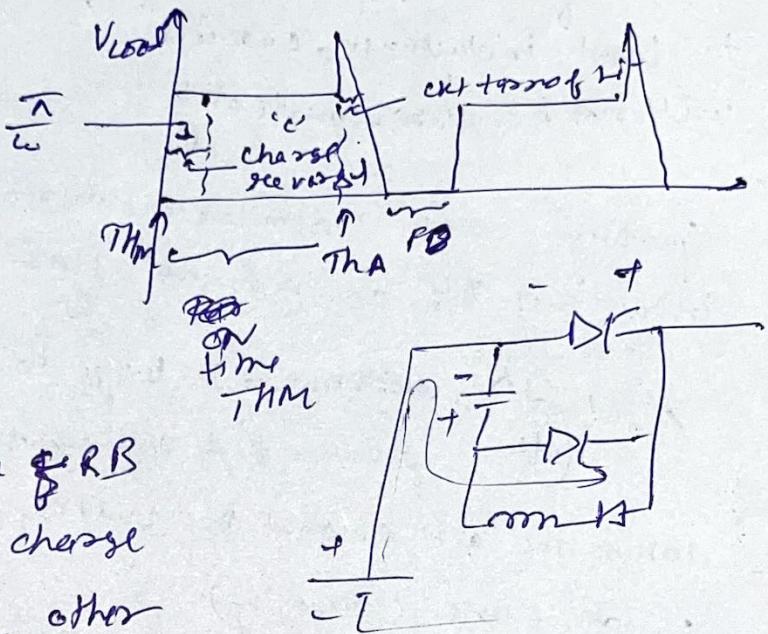• I path  $\rightarrow E \rightarrow C \rightarrow T_{HA} \rightarrow$  load No  $\leftrightarrow$  charge but  $T_{HM}$  is still  $R_B$  &  $V_L > 0$  after some time






## Thyristor commutation

C-charged to E by source voltage

$T_{hM} \rightarrow ON$

current path A-D-L (C Ckt)

so we get LC oscillation

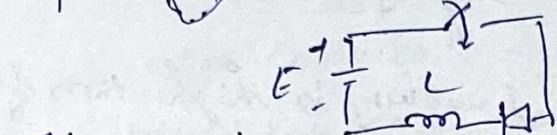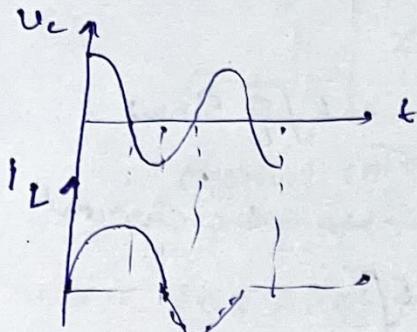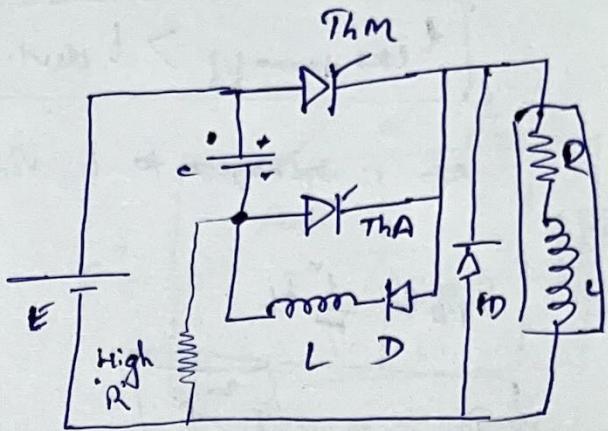

This ckt is for charge reversal - it cycle will not occur due to Diode.

$$\omega = \frac{1}{\sqrt{LC}}$$


$$T_{ON(M)} \geq \frac{\pi}{\omega} \left( \text{charge reversal time} \right)$$

$T_{hM} \rightarrow ON \rightarrow$  charge reversal factor,

As  $ThA \rightarrow ON$

$T_{hM} \rightarrow OFF(RB)$

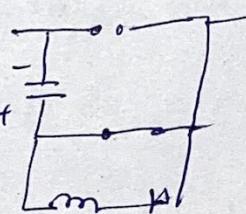Current  $\rightarrow E - C - ThA - \text{load}$




$$V_{Load} = E + U_C$$

$$CE = I \times t_{off} - t_{on/off}$$

$I =$  Load current at the time of commutation

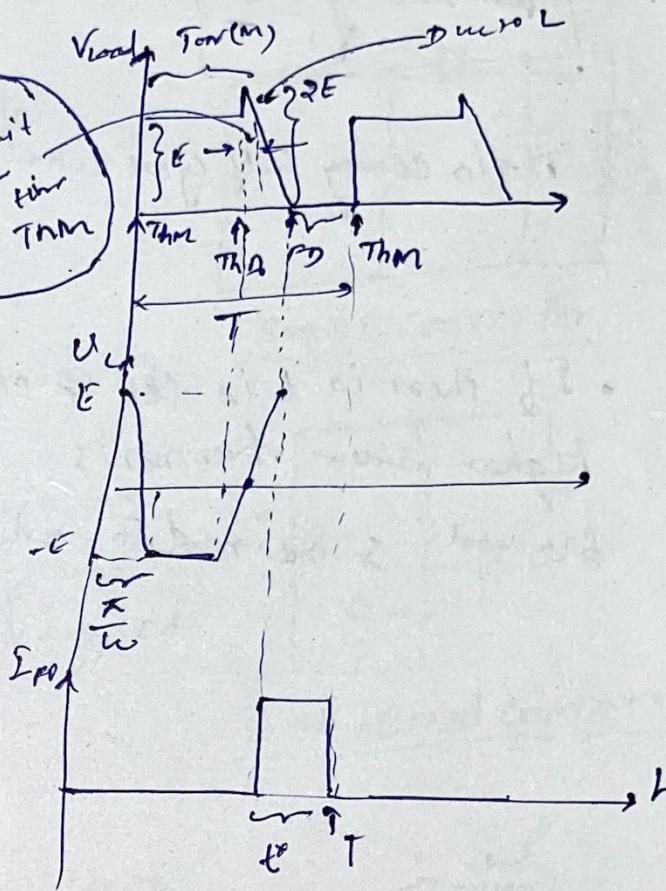$\hookrightarrow$  constant [if chopping freq is high]



$$t_{(kt+\theta)on} > t_{(k+1)t+\theta}off \rightarrow \text{defined by manufacturer}$$


around 80 MS

As C charges to E when  $\omega_D t$  goes a little  $\Rightarrow I_D = P_D \rightarrow 0$   
or  $V_D > E$

$$I_{D0} = \frac{t^* I_L}{T}$$

$$\text{forms } = \sqrt{I_L^2 + \frac{t^*}{T}}$$

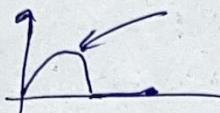$I_D$  is carrying half cycle current only



$E_C$  Sinwt  
 $I_C$  current


$$= \sqrt{I_L^2 + E_C^2}$$

- If there is  $L$  in coil & chopping frequency is high then for higher order harmonics  $\omega_L$  is high it is automatically blocked so no need to add additional inductor in  $C_L$ .

16/09/2022
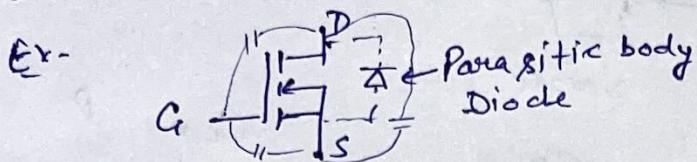
## • DC to DC Converter

- SW Consider is Gate controlled  
(both turn ON & turn off through Gate to Source voltage)



'n' channel enhancement mode  
MOSFET


when  $V_{DS} > V_{GS}/\text{threshold}$

SW. Conducts.

$|V_{GS}| < 20 \text{ V}$  {In normal Power MOSFET?}


if  $V_{GS} \rightarrow V_{DS} \downarrow$  two losses  
① conduction loss  
② switching loss

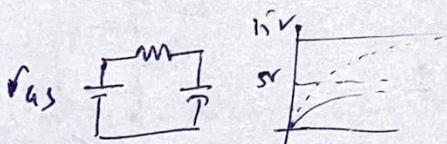- $I_{GTO}$  but charging current is to be supplied to turn on mosfet



• LC oscillation may happen due to inherent inductor

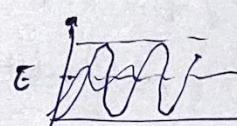• if undamped CCR  $V_{DS} = E$   
undamped case




• so we put R in series of 1st stage inductance to clamp LC oscillator


• higher the distance  $\Rightarrow$  Higher the inductance

$$L_I = \phi$$

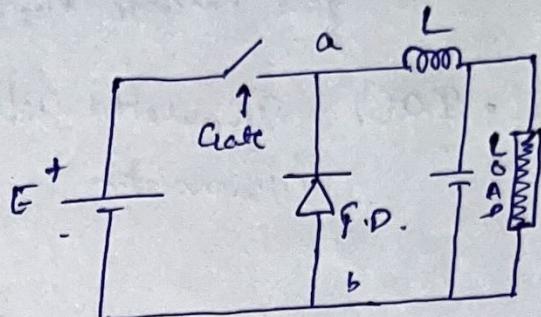
- If they are close ① & ② cancels and we minimize the inductance. also by twisting wires.





Buck Converter (Chopper)

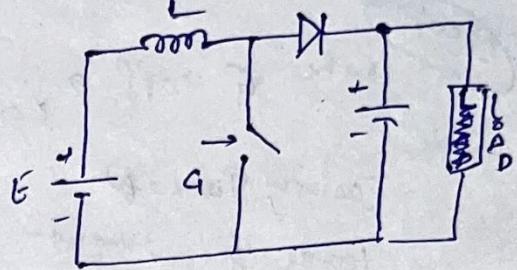



Boost Converter

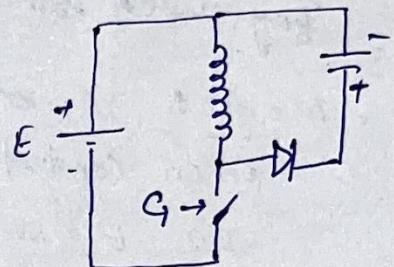

Buck/Boost converter

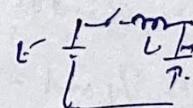
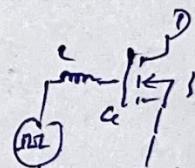


to clamp LC oscillator

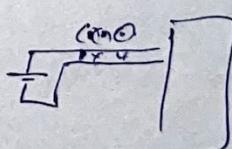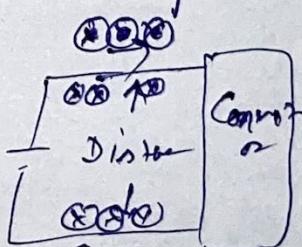

During Turnoff if  $V_G = 0$  slow turnoff  
to fast Turnoff  $V_{GS} = -V_0$

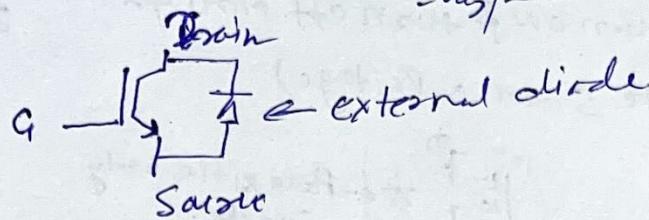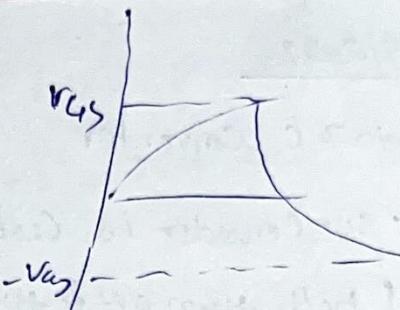- IABT: Insulated Gate Bipolar junction transistor





B cut

when  $G \rightarrow \text{off}$   $\Rightarrow$  appears at  $C_{DS}$  & blocked

During Turnon

large  $I$  is sequen-  
tial for large  $V_D$

$I_{Dg}$  will be small

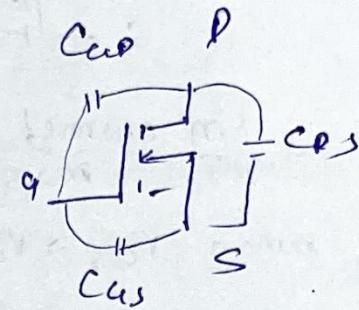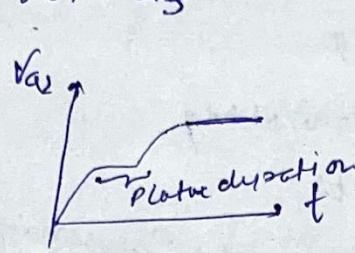

- Model 1 SWON

when control ch is on

$I \rightarrow E \rightarrow SW \rightarrow L \rightarrow \text{Load}$




- Model 2 SW OFF

$I \rightarrow L \rightarrow \text{Load} \rightarrow FD$

$$S \text{ or } \gamma = \frac{t_{on}}{T}, 0 < S < 1$$

- Model 3 C → OFF, FD → OFF

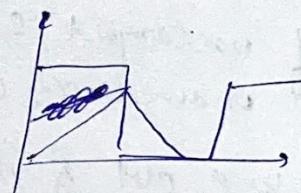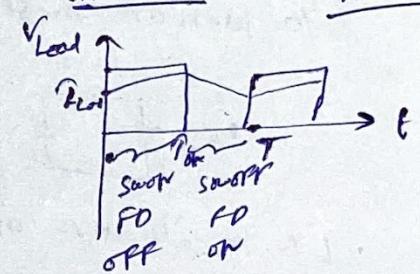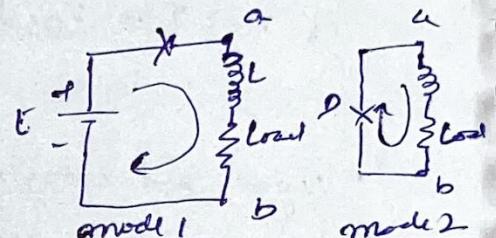$I_{\text{load}} = 0$  i.e. discontinuous



22/09/22

• DC to DC Boost Converter


under steady state condition  
inductor current  
and continuous current

2 modes of operation:

mode 1 when  $s_w$  is on form

$$0 < t < t_{on}, \quad D \text{ is R.B. } \{ \text{because } V_o > E \}$$


eq. ckt.

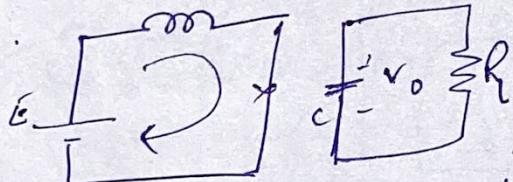


i<sub>L</sub> builds linearly.

$$V_o \approx V_c$$

ideal cat elements.

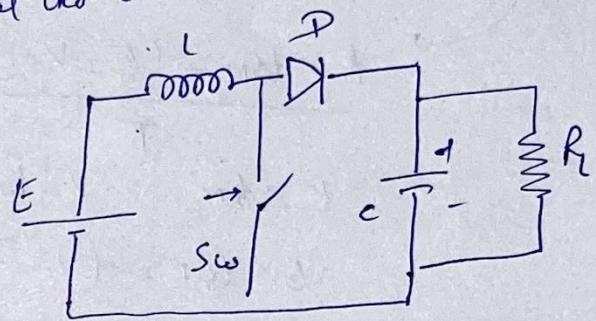
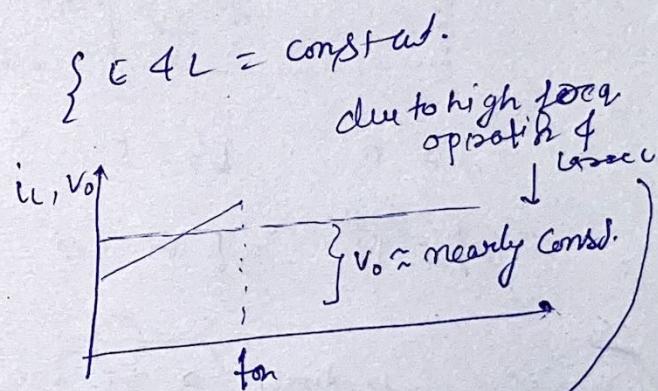
$$\therefore E = L \frac{di}{dt} \quad \{ E \propto L = \text{constant.}$$



{ in high freq,  $\omega \rightarrow \infty$   
C does not discharge  
immediately }

Mode 2 starts with turning off of 'sw'  
 $t_{on} < t < T$



$$e_L = L \frac{di}{dt} = E - V_0 ,$$

If  $V_0 \approx \text{constant}$ . linear fall of  
 $i_L$ .

$$e_L \text{ avg over } T' = 0$$

$$e_L = L \frac{di}{dt}$$

$$i_C = C \frac{dv}{dt}$$

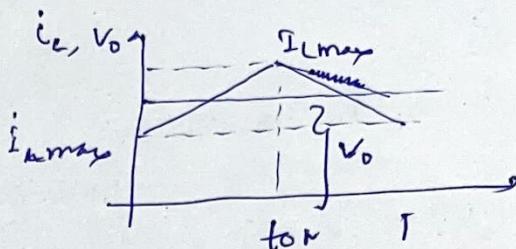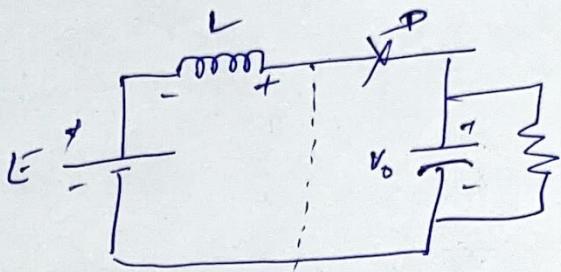

$$\frac{Ex t_{on} + (E - V_0) t_{off}}{T} = 0$$

$$Ex t_{on} = V_0 t_{off} - E t_{off}$$

$$Ex t_{on} = (V_0 - E)(T - t_{on})$$

$$Ex t_{on} \neq E t_{off} = V_0 (T - t_{on})$$

$$ExT = V_0 (T - t_{on})$$

$$(1 - \frac{t_{on}}{T}) V_0 = E$$

$$V_0 = \frac{E}{1 - \delta}$$

$$0 < \delta < 1$$



$\delta = 0 \quad V_0 = E \quad \left\{ \text{Cap. charged to } E \text{ always} \right\}$   
 $\delta = 1 \quad sw \text{ is always on}$

Cap. electrolyt.  $\Rightarrow$  DC

charging discha



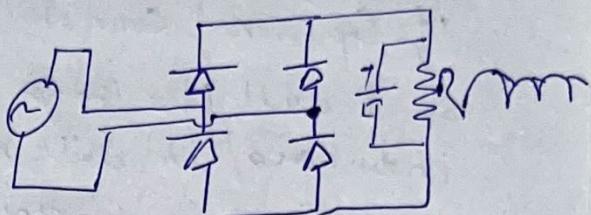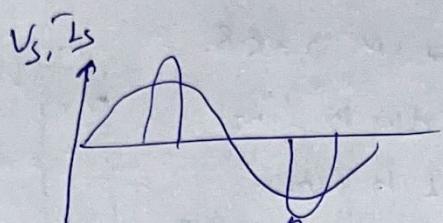so AydC<sub>0</sub> but Ay acts as  $\sim$  (current source)




$I_s$  peaks  
due to  $C \rightarrow 0$  & D conducts for small time

So harmonics

- Buck boost converter:

$$\text{Mode 1} \Rightarrow S_w = \text{ON}, V_L = E$$
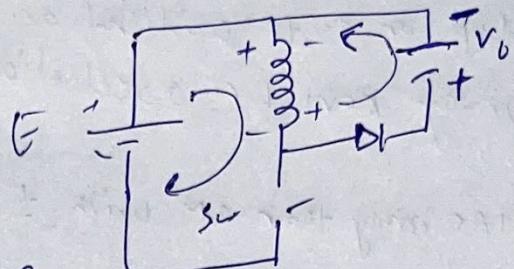
$$\text{Mode 2} \Rightarrow S_w = \text{OFF}, V_L = -V_o$$



$$E_{avg} = 0 = \frac{E \times t_{on} - V_o \times t_{off}}{T}$$


$$E \times t_{on} = V_o (T - t_{off})$$

$$V_o = \frac{E}{(T - t_{off})} \left( \frac{t_{on}}{T} \right)$$

$$V_o = E \left[ \frac{s}{1-s} \right]$$

26/09/2022


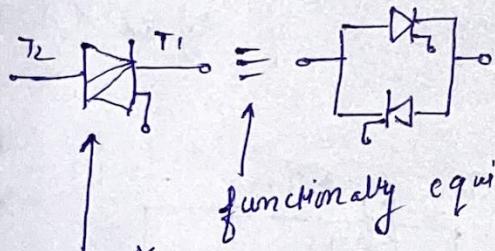
- 1φ AC to AC conversion using phase angle control



functionally equivalent

cheaper  
but inferior characteristics  
especially  $\frac{dV}{dt}$  rating

$$\frac{dV}{dt} < 5V/\mu\text{sec}$$

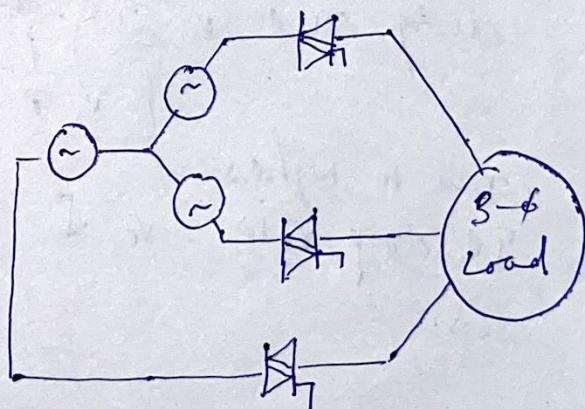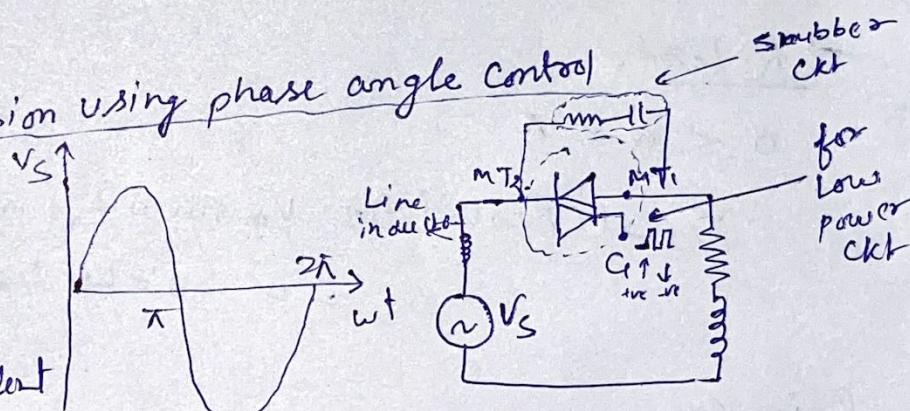


3-φ TRIAC Control Ckt

If Cap is not connected, if  $T \rightarrow 0$ ,  $I \rightarrow R \cdot B$ .

So  $I$  will flow through  $T$  but due to line inductance it will not let  $I$  to flow.

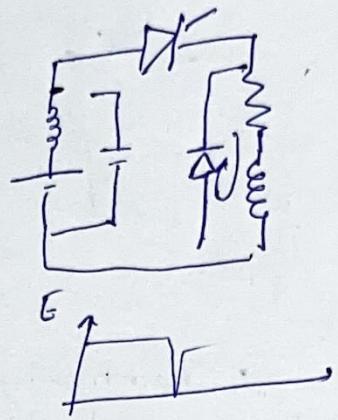
So Now  $T$  is turning on &  $D$  is ~~turning~~ off so we connect Cap. It will supply the current when  $I$  is building in  $L$  & voltage dip or surge will not occur. But there may have LC oscillations



- TRIAC may turn on with  $\pm I_g$  &  $\pm M_{T1}, M_{T2}$

But it is more sensitive to  $+M_{T2}$  &  $-M_1$ , with  $+V_R I_g$  (i.e. less  $I_g$  is required). & more sensitive to  $+M_{T1}$  with  $M_{T2}$  with  $-V_R I_g$ .

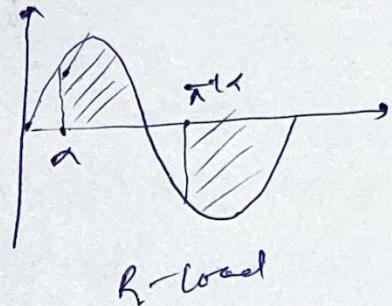→ fundamental & component of higher order harmonics. in motor wave.




→  $R_{load}$ .

$$0 < \alpha < \pi$$

$$V_{load}(\text{resistive}) = V_m \sin \omega t, \quad \alpha < \omega t < \pi \quad \left\{ \text{for half cycle} \right\}$$


$$= 0 \quad 0 < \omega t < \alpha$$

firing  $C_{th}$ .

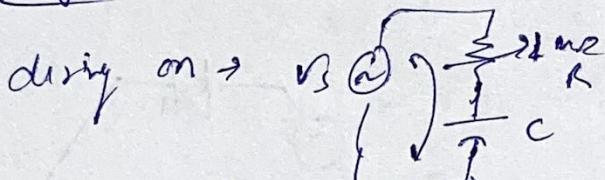

During on  $\rightarrow V_S$   $\downarrow$   $V_C$   $\downarrow$   $\Rightarrow I_R$   $\downarrow$   $V_C$   $\downarrow$   $V_S$

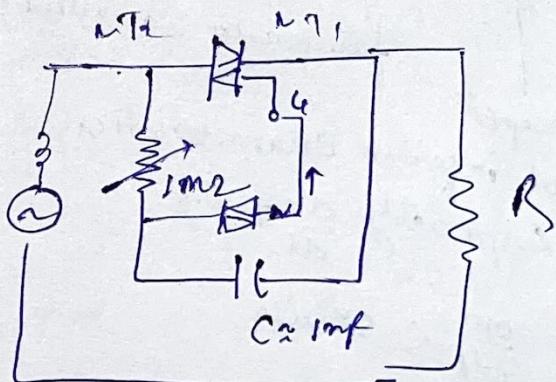Due to higher  $I_R$  drop  $V_C$  is less.



- when  $V_C$  is less DIAC is off.  
It blocks  $V_C$  upto  $\pm V_{B0}$
- As  $V_C > V_{B0}$ ,  $V_{Diac}$  starts to drop & starts to conduct. sudden drop in diac but cap does not allow it so

$$V_C = V_{B0} \text{ and } V_{Diac} \approx 10V \text{ (let)}$$

so current flows b/w DIAC  $\Rightarrow$  a  $\Rightarrow P N$  junctions. during ON  
some thing happens  $\rightarrow$  cycle in opposite direction.

- when TRIAC is on it is like shot in RC charging down  
or vice. it starts to discharge with small current without affecting the I forward in TRIAC.

